

# Engr098 Lab7

Vincent Liu

**Circuit and convention.** Current source  $I_s = 6$  A feeds a top node. A  $2\Omega$  resistor is from that node to ground (left branch). Through a switch, the node also connects to a  $4\Omega$  resistor in series with an inductor  $L = 3$  H to ground (right branch). The inductor current  $i(t)$  is defined *downward* through  $L$ .

At  $t = 0$  the switch *closes*. Thus:

$$i(t) = \begin{cases} i(0^-), & t < 0, \\ i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau}, & t \geq 0. \end{cases}$$

## 1. Initial current $i(0^-)$

For  $t < 0$  the switch is *open*, so the RL branch is disconnected; no steady DC path exists through  $L$ . Therefore,

$$\boxed{i(0^-) = 0 \text{ A}}, \quad \Rightarrow \quad i(0^+) = i(0^-) = 0 \text{ A}.$$

(For reference, the left node voltage is  $V = I_s R = 6 \times 2 = 12$  V with only the  $2\Omega$  to ground.)

## 2. Final (steady) current $i(\infty)$

For  $t \rightarrow \infty$  with the switch closed, the inductor is a short. The right branch becomes a  $4\Omega$  to ground in parallel with the  $2\Omega$  to ground.

$$R_{\parallel} = 2 \parallel 4 = \frac{2 \cdot 4}{2 + 4} = \frac{4}{3} \Omega, \quad V_{\text{node}} = I_s R_{\parallel} = 6 \cdot \frac{4}{3} = 8 \text{ V}.$$

Hence the DC current in the right branch (and through the inductor) is

$$\boxed{i(\infty) = \frac{V_{\text{node}}}{4} = \frac{8}{4} = 2 \text{ A}}.$$

## 3. Time constant $\tau$

With the switch closed, find the Thevenin resistance seen by  $L$  with independent sources killed (current source opened). Looking into the inductor terminals, the path to ground is

$$R_{\text{th}} = 4 \Omega + 2 \Omega = \boxed{6 \Omega}.$$

Thus

$$\boxed{\tau = \frac{L}{R_{\text{th}}} = \frac{3}{6} = 0.5 \text{ s}}.$$

## 4. Complete response

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 2 + (0 - 2)e^{-t/0.5} = 2(1 - e^{-2t}) \text{ A}, \quad t \geq 0.$$

**Checks.**  $i(0^+) = 2(1 - 1) = 0$  A (continuous at  $t = 0$ ).  $i(\infty) = 2(1 - 0) = 2$  A matches the DC analysis.

**(Optional) Inductor voltage.** With the passive sign convention (voltage drop top to bottom on  $L$ ):

$$v_L(t) = L \frac{di}{dt} = 3 \cdot (4e^{-2t}) = \boxed{12e^{-2t} \text{ V}}, \quad t \geq 0.$$

**Plot tip.** In Desmos/PSPICE, use  $i(t) = 2(1 - e^{-2t})$  for  $t \geq 0$ ; a time window of  $0 \leq t \leq 2.5$  s ( $= 5\tau$ ) shows the full rise.